

GOVERNMENT POLYTECHNIC, BHADRAK
DEPARTMENT OF ELECTRICAL
INTERNAL ASSESSMENT 2022 (3RD SEMESTER)
Sub: Circuit & Network Theory (Th-II)

F.M.: 20


Time: 1 Hour

QUESTION NO.1 AND NO.2 ARE COMPULSORY


1.

[2×5 = 10]

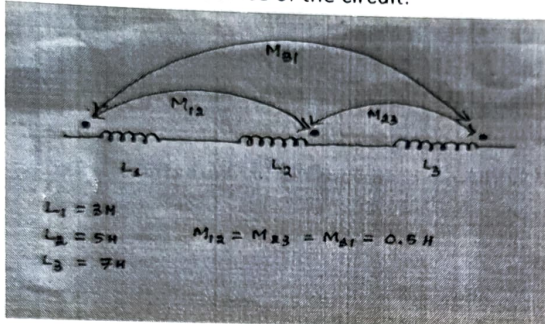- a) Write the statement of superposition theorem.
- b) Draw Thevenin's equivalent circuit and norton's equivalent circuit.
- c) What is co-efficient of coupling .Write the relationship between self inductance, mutual inductance and co-efficient of coupling.
- d) Find the total inductance of the circuit.



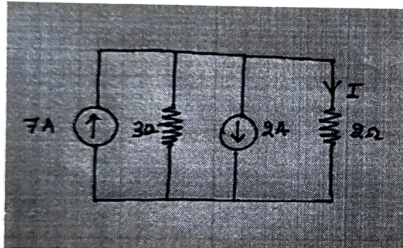- e) Find the power dissipated in 2Ω resistor.




- 2 . Write short note on B-H curve. What is hysteresis loop?

[5]

3. Using maximum power transfer theorem , find maximum power transferred to the load resistance R_L

[5]

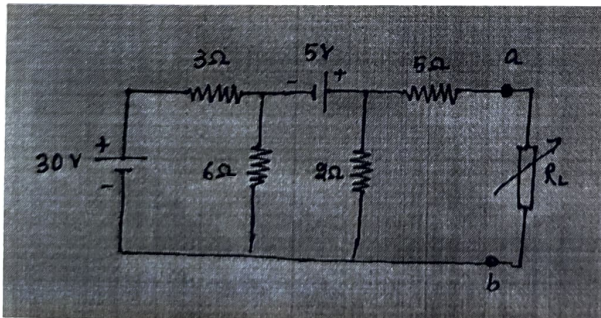

4. Draw Thevenin's equivalent circuit between terminal 'a' and 'b' of the above figure.

[5]